

Week 5

① half adder


a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

a \ b	0	1
0	0	1
1	1	0

sum
 $a\bar{b} + \bar{a}b$
 $a \oplus b$

a \ b	0	1
0	0	0
1	0	1

carry
 ab
 $a \cdot b$

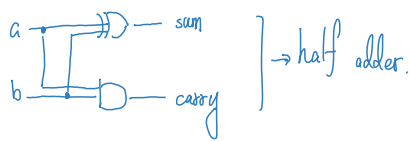

② full adder

a	b	c _{in}	sum	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

a \ b c _{in}	00	01	11	10
0	0	1	1	0
1	1	0	0	1

sum

a \ b c _{in}	00	01	11	10
0	0	0	1	0
1	0	1	1	1



cout

$$\begin{aligned} & \bar{a}\bar{b}c_{in} + \bar{a}b\bar{c}_{in} + a\bar{b}\bar{c}_{in} + ab c_{in} \\ &= c_{in}(\bar{a}\bar{b} + ab) + \bar{c}_{in}(\bar{a}b + a\bar{b}) \\ &= c_{in} \cdot (a \oplus b) + \bar{c}_{in} (a \oplus b) \\ &= (a \oplus b) \oplus c_{in} \end{aligned}$$

$$\begin{aligned} & b c_{in} + a c_{in} + ab \\ &= (a \cdot b) + (a \oplus b) \cdot c_{in} \end{aligned}$$

推倒 模数 不推倒


拆解 Full Adder 为 2 个 Half Adder

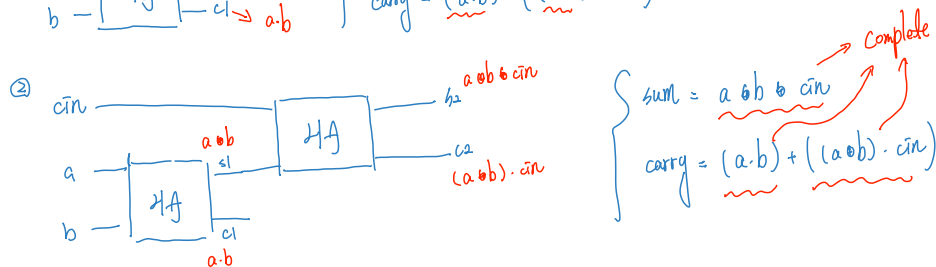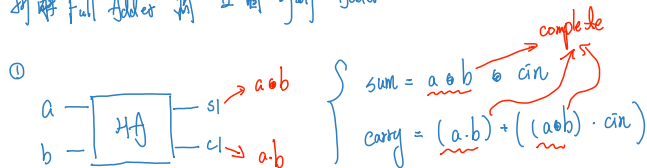

可以这样 $\text{sum} = \underbrace{a \oplus b}_{s1} \oplus c_{in}$

跟 cin xor 的话 1 有进位所以拿 1 试试看。

③

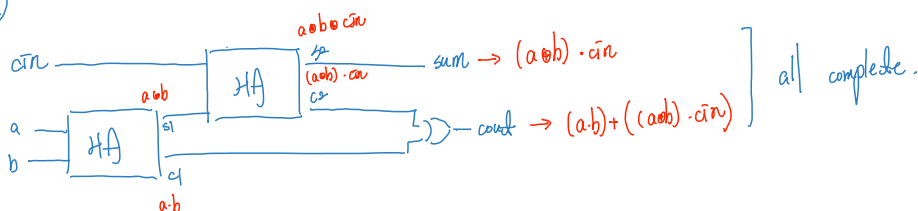

Week 11

1 Hz \Rightarrow 每秒 1 個週期

50 MHz $\Rightarrow 50 \times 10^6$ Hz \Rightarrow 每秒 50×10^6 個週期

50 MHz $\Rightarrow \frac{1}{50 \times 10^6}$ s/次 (週期)

$$\frac{1}{50 \times 10^6} = \frac{1}{5 \times 10^7} = 0.2 \times 10^{-7} = 2 \times 10^{-8} = 20 \times 10^{-9} = 20 \text{ ns}.$$

$$20 \text{ ns/次} \rightarrow 1 \text{ s/次}$$

Time Expire \Rightarrow 每秒 0.5 秒的週期數

$$\frac{50 \times 10^6}{2} = 25 \times 10^6 \text{ 次}.$$

而 frequency divider 就是將 N Hz \rightarrow 1 Hz.

$$N \text{ Hz} \rightarrow N \text{ 次/秒}$$

而 Time Expire 為每秒 0.5 秒的週期數

$$\text{次 } \frac{N}{2} \text{ 次/0.5 秒}$$

week 12.

moore finite state machine.

