



LAB - 08

陳培殷老師

國立成功大學 資訊工程系


YOUTUBE

[HDL Part 6 上\(影片 9:50\)](#)

[HDL Part 6 下\(影片 11:49\)](#)

Sequential Circuit (1/3)

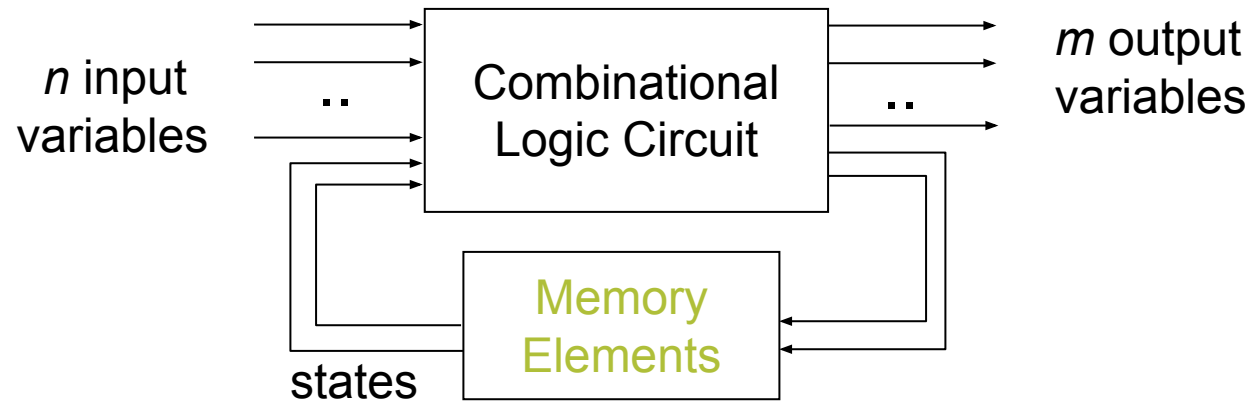A sequential circuit is a system whose outputs at any time are determined from the present combination of inputs and the previous inputs or outputs.



- Sequential components contain memory elements
- The output values of sequential components depend on the input values and the values stored in the memory elements

Sequential Circuit (2/3)

```
1 module sequential_circuit(clk, reset);
2 input clk, reset;
3
4 always@(posedge clk or negedge reset)
5 begin
6
7     if(!reset)
8     begin
9         // Initialization
10    end
11    else
12    begin
13        // Circuit functionality
14    end
15
16 end
17
18 endmodule
19
```

正緣同步電路

低位準非同步重置

Sequential Circuit (3/3)

■ Blocking statement vs nonblocking statement

```
27 module combinational_circuit(in, a, b);
28
29 input in;
30 output reg [3:0] a,b;
31
32 input in;
33 output reg [3:0] a,b;
34
35 always@(*)
36 begin
37
38     if(in == 0)
39     begin
40         a = 4'h1;
41         b = 4'hf;
42
43         a = b; // a -> 4'hf
44         b = a; // b -> 4'hf
45     end
46     else
47     begin
48         a = 4'h1;
49         b = 4'hf;
50
51         b = a; // b -> 4'h1
52         a = b; // a -> 4'h1
53     end
54
55 end
56
57 endmodule
```

```
1 module sequential_circuit(clk, reset);
2 input clk, reset;
3
4 reg [3:0] a,b;
5
6 always@(posedge clk or negedge reset)
7 begin
8
9     if(!reset)
10    begin
11        a <= 4'h1;
12        b <= 4'hf;
13    end
14    else
15    begin
16        a <= b; // a -> 4'hf
17        b <= a; // b -> 4'h1
18    end
19
20 end
21
22 endmodule
```


Lab I (1/3)

■ 請設計一個具備下列功能的計數器：

- 正緣同步電路，**低位準非同步** 重置
- 當reset訊號為0，將計數器歸零，輸出維持 0
- 當reset訊號為1，且enable訊號為1：
 - 1) up_down = 0 , **每秒計數減 1**
 - EX: 0 -> F -> E -> -> 2 -> 1 -> 0 -> F
 - 2) up_down = 1 , **每秒計數加 1**
 - EX: 0 -> 1 -> 2 -> -> E -> F -> 0 -> 1
- 當enable訊號為0時，保持目前數 值不變，**暫停計數**。
- FPGA版之clock頻率為50MHz，需藉由除頻器將 clock訊號降為 1Hz
 - 實現方式為透過一個計數器，計算經過幾個 **時脈正緣**，當計數到 50×10^6 即代表經過一秒

Lab I (2/3)

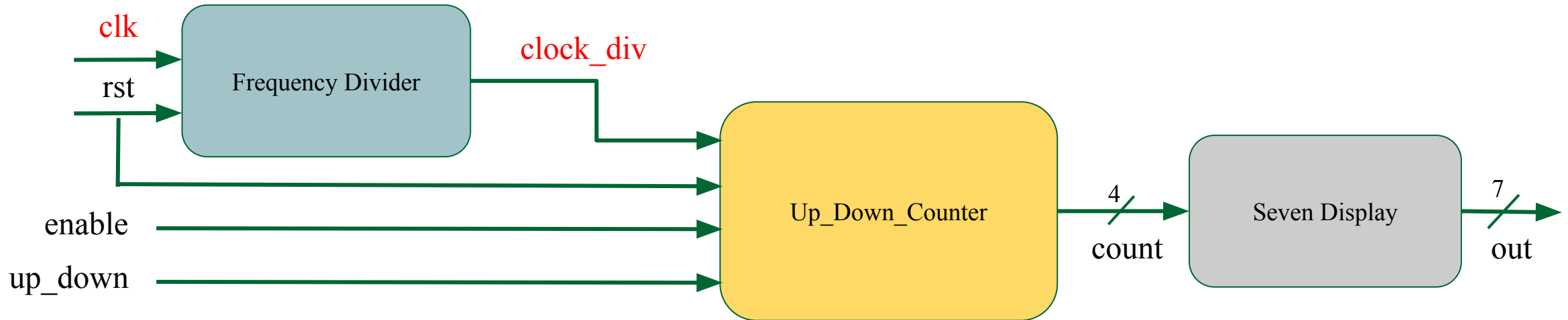
- 請將計數的數值顯示於七段顯示器
- 系統架構圖請參考下方
 - ❑ Input : clk(**MAX10_CLK1_50**) , rst(SW0), up_down(SW1), enable(SW2)
 - ❑ Output : out(7 bits, HEX06~HEX00)
- 可使用structural description設計, 其中, 除頻器及計數模組為循序電路, 七段顯示器控制模組則為組合電路




Lab I (3/3)

■ 輸出範例 (rst=1, enable=1)

1) up_down = 0

 

2) up_down = 1

 

Lab I (3/3)

■ 狀態範例：

rst(SW0)	up_down(SW1)	enable(SW2)	輸出結果
0	0	0	維持輸出0
0	0	1	維持輸出0
0	1	0	維持輸出0
0	1	1	維持輸出0
1	0	0	暫停在當前狀態 (ex. 下數狀態。如果數到3, 就停在3)
1	0	1	倒數(0->f->e...->1->0->f)
1	1	0	暫停在當前狀態 (ex. 上數狀態。如果數到5, 就停在5)
1	1	1	上數(0->1->2....->e->f->0)

Lab - Hint(1/3)

- Frequency Divider (sequential circuit)

- 將clock頻率從50MHz降為1Hz

- Counter (sequential circuit)

- 加/減計數器模組, 支援 enable 控制暫停功能

- Seven Display (combinational circuit)

- 將Counter數值轉為七段顯示器控制訊號

- Module呼叫範例 (Structural description)

- **FrequencyDivider** u_FreqDiv (.clk(clk), .rst(rst), .clk_div(clk_div));
- **Counter** u_counter(.clk(clk_div), .rst(rst), .up_down(up_down), .enable(enable), .count(count));
- **SevenDisplay** u_display(.in(count), .out(out));

```
module_name unit_name(.port_name(signal_name),.port_name(signal_name).....)
```

Lab – Hint(2/3)

■ 除頻器範例：

要達到產出1Hz的div_clk,
要每**0.5秒**flip一次div_clk。

```
1  `define TimeExpire 32'd[REDACTED]
2
3  module clk_div(clk,rst,div_clk);
4  input clk,rst;
5  output div_clk;
6
7  reg div_clk;
8  reg [31:0]count;
9
10 always@(posedge clk)
11 begin
12     if(!rst) 低位準同步reset
13     begin
14         count <= 32'd0;
15         div_clk <= 1'b0;
16     end
17     else
18     begin
19         if(count == `TimeExpire)
20         begin
21             count <= 32'd0;
22             div_clk <= ~div_clk;
23         end
24         else
25         begin
26             count <= count + 32'd1;
27         end
28     end
29 end
30
31 endmodule
```

Lab - Hint(3/3)

```
always@(in)
begin
    module SevenDisplay(in,out);
        case(in)
            4'd0: out = 7'b1000000;
            4'd1: out = 7'b1111001;
            4'd2: out = 7'b0100100;
            4'd3: out = 7'b0110000;
            4'd4: out = 7'b0011001;
            4'd5: out = 7'b0010010;
            4'd6: out = 7'b0000010;
            4'd7: out = 7'b1111000;
            4'd8: out = 7'b0000000;
            4'd9: out = 7'b0010000;
            4'd10: out = 7'b0001000;
            4'd11: out = 7'b0000011;
            4'd12: out = 7'b1000110;
            4'd13: out = 7'b0100001;
            4'd14: out = 7'b0000110;
            default: out = 7'b0001110;
        endcase
    end
endmodule

always@(in)
begin
    case(in)
        4'd0: out = 7'b1000000;
        4'd1: out = 7'b1111001;
        4'd2: out = 7'b0100100;
        4'd3: out = 7'b0110000;
        4'd4: out = 7'b0011001;
        4'd5: out = 7'b0010010;
        4'd6: out = 7'b0000010;
        4'd7: out = 7'b1111000;
        4'd8: out = 7'b0000000;
        4'd9: out = 7'b0010000;
        4'd10: out = 7'b0001000;
        4'd11: out = 7'b0000011;
        4'd12: out = 7'b1000110;
        4'd13: out = 7'b0100001;
        4'd14: out = 7'b0000110;
        default: out = 7'b0001110;
    endcase
end
endmodule
```

Notice

- 請勿命名中文或數字開頭的資料夾
- Device family 請確認與 FPGA Chip 符合 (**10M50DAF484C7G**)
- Top module name & Top entity name 需要一致
- 在組合電路中, case、if...else...若沒有寫滿, 合成後會產生latch